

Pipelined 32-bit Prefix Adder Workflow

Input Breakdown:

- Inputs are two 32-bit binary numbers: $A[31:0]$ and $B[31:0]$.
 - A carry-in (C_{in} , typically 0) may also be included.
-

Step 1: Generate and Propagate Signals:

- Compute **Generate (G)** and **Propagate (P)** signals for each bit: $G[i] = A[i] \cdot B[i]$ (Carry generated by bit i)
 $G[i] = A[i] \cdot B[i]$ (Carry generated by bit i)
 $P[i] = A[i] \oplus B[i]$ (Carry propagated by bit i)
 $P[i] = A[i] \oplus B[i]$ (Carry propagated by bit i)
-

Step 2: Pipeline Stage 1 - Initial Combination:

- Group adjacent bits to compute intermediate generate and propagate signals:
 $G'[i] = G[i] + (P[i] \cdot G[i-1])$
 $G'[i] = G[i] + (P[i] \cdot G[i-1])$
 $P'[i] = P[i] \cdot P[i-1]$
 $P'[i] = P[i] \cdot P[i-1]$
 - Store results in pipeline registers for further processing.
-

Step 3: Pipeline Stage 2 - Group Propagation:

- Combine results from Stage 1 to compute wider groups (e.g., 4-bit or 8-bit blocks):
 $G''[i] = G'[i] + (P'[i] \cdot G'[i-2])$
 $G''[i] = G'[i] + (P'[i] \cdot G'[i-2])$
 $P''[i] = P'[i] \cdot P'[i-2]$
 $P''[i] = P'[i] \cdot P'[i-2]$
 - Use pipeline registers to hold these intermediate values.
-

Step 4: Final Carry Calculation:

- Continue combining blocks in subsequent pipeline stages until all carries ($C[i]$) are computed.
-

Step 5: Compute the Sum:

- Calculate the sum for each bit using the propagate signals and computed carries:
 $S[i] = P[i] \oplus C[i-1]$
 $S[i] = P[i] \oplus C[i-1]$
-

Output Assembly:

- Combine the sum bits ($S[31:0]$) for the final 32-bit sum.
 - The carry-out from the final stage ($C[32]$) indicates overflow.
-

Pipeline Stages:

- Intermediate results (G , P , and C) are stored in registers between stages to ensure high throughput.